TOSHIBA

Magnetic Amplifier Regulation of Switch Mode Power Supplies

Basic Design of Saturable Reactors

A Magnetic Amplifier (or "Mag-Amp") is a post regulation method utilizing a saturable reactor (wirewrapped saturable core). It regulates the auxiliary outputs of a switching power supply by delaying the rise in voltage of a PWM pulse. In this note, the basic design of a Mag-Amp will be discussed.

The transformer secondary voltage should allow, after Pulse Width Modulation, for an additional 20% (i.e. "headroom") over the desired main output voltage:

$$V_{s} \cdot (T_{ON} / T) = 1.2 \cdot V_{1}$$
 (1)
where:
 $V_{s} = Transformer Secondary Voltage$

 $V_s =$ Main Output Voltage

For the auxiliary output, the Mag-Amp delays the rise in the voltage pulse by an amount ΔT . Hence the auxiliary output voltage, V₂, plus headroom is given by:

> $V_{s} \cdot ((T_{ON} - \Delta T) / T) = 1.2 \cdot V_{2}$ (2) where:

 V_2 = Auxiliary Output Voltage

 ΔT = Delay time (see the figure below)



The magnetic flux blocked by the Mag-Amp, Φ , is the shaded area above:

$$\Phi = V_s \cdot \Delta T \quad [Wb] \tag{3a}$$

Substituting Equations (1) and (2) into Equation (3a): $\Phi = 1.2 \cdot (V_1 - V_2)/f$ (3b)

where:

f = Switching Frequency = 1 / T

For the Mag-Amp to regulate the circuit, the magnetic flux of the Mag-Amp must be at least that obtained in Equation 3:

$$N \cdot \Phi_{C} \ge \Phi$$
 (4)
where:
N = Number of turns of wire

 $\Phi_{\rm C}$ = Flux in Saturable Core

Another necessary requirement for a Mag-Amp is that the area available in the core for wire winding be at least the area of the required windings:

	$A_{W} \cdot K_{W} \geq N \cdot A_{Wire}$	(5)
where:		
$A_w =$	Core winding area [mm ²]	

 K_w = Winding factor (typical value = 0.4)

A_{wire} = Cross-Sectional area of the wire [mm²]

The following is obtained from Conditions 4 & 5:

 $\Phi_{C} \cdot A_{W} \ge \Phi \cdot I_{S} / (K_{W} \cdot J) \quad [Wb \cdot mm^{2}]$ (6) where:

 $I_s =$ Auxiliary Output Current

J = Average Current Density [A/mm²]

The appropriate core is selected by calculating the Right Hand side of Condition 6 and comparing the result to the values of $\Phi_C A_W$ for saturable cores. Usually the smallest core fulfilling Condition 6 is selected. Table 1 (on the reverse side) lists these values for Toshiba's MS Series of Amorphous Magnetic Saturable Cores.

Once a core is selected, the number of turns, N, in the winding for the saturable reactor can be obtained by rearranging Condition 4:

$$N \ge \Phi / \Phi_C \quad [turns] \tag{7}$$

where:

 $\Phi_{\rm C}$ = Magnetic flux of the core selected.

The diameter of the winding wire, d, is:

$$d \ge 2 \cdot (I_s / \{\pi \cdot J\})^{0.5} \text{ [mm]}$$
(8)

Conditions 6 - 8 determine the basic design of a Mag-Amp. However, specific circuit conditions may indictate other selections be used.

EXAMPLE

Design a Mag-Amp to regulate an auxiliary output voltage of 5V and output current of 4A. The main output voltage is 12V and the switching frequency is 200kHz.

For an auxiliary output voltage $V_2 = 5V$; a main output voltage $V_1 = 12$ V; and frequency f = 200 kHz; the required magnetic flux, from Equation (3b), for regulation should be:

 $\Phi = 1.2 \text{ x} (12 \text{V} - 5 \text{V}) / (200,000 \text{ Hz}) = 42 \,\mu\text{Wb}$

For an output current $I_s = 4A$; assuming an average current density of $J = 5 \text{ A/mm}^2$; Condition 6 leads to:

 $\Phi_{\rm C} \cdot A_{\rm w} > 42 \ {\rm x10^{-6} \ Wb} \ {\rm x4A} \ / \ (0.4 \ {\rm x5A/mm^2})$

> 84 μ Wb·mm²

Therefore, from Table 1, Toshiba Amorphous Saturable Core MS 10x7x4.5W is selected.

From Table 1, the total magnetic flux, Φ_c , of an MS 10x7x4.5W core is 4.73 µWb. From Condition 7 the number turns of the coil, N, of the saturable reactor is obtained:

N ≥ 42 x10⁻⁶Wb / (4.73 x10⁻⁶Wb) = 8.9 \therefore N = 9 turns

The winding wire diameter, d, is determined from Condition 8:

$$d \ge 2 \times (4/\{\pi \ge 5\})^{0.5} = 1.00 \text{ mm}$$

 $\therefore d = 1 \text{ mm is selected}$

To regulate this output, use an MS 10x7x4.5W core with 9 turns of 1 mm wire.

	C	ore S	ize	Cross-Sectional	Magnetic	Total	•
Part Number			Height	Arca [mm ²]	Path Length	Flux	
MS 7x4x3W							
MS 9x7x4 <i>.</i> 5W	9	7	4.5			3.16	72
MS 10x7x4.5W	10	7	4.5			4.73	96
MS 10x6x4.5W	10	6	4.5	6.75		6.31	
MS 12x8x3W	12	8		4.50		4.20	119
MS 12x8x4.5W	12	8	4.5	6.75		6.31	
MS 14x8x4.5W	14	8	4.5			9.47	
	• •	10	2	5 63	30 3	5 26	264
MS 15x10x3W	ID	IV			***********		

Table 2 is provided as an approximate guide to select a Mag-Amp. It is intended to be used ONLY as Guide.

			`able 2 ion Guide (200 kHz)	
Forward Converter				
		2 Amps	4 Amps	8 Amps
Output	1 V	MS 8x7x4.5W - 4 Turns	MS 8x7x4.5W - 4 Turns	MS 8x7x4.5W - 4 Turns
Voltages	3 V	MS 8x7x4.5W - 11 Turns	MS 9x7x4.5W - 6 Turns	MS 10x7x4.5W - 4 Turns
Difference	5 V	MS 8x7x4.5W - 19 Turns	MS 9x7x4.5W - 9 Turns	MS 12x8x4.5W - 5 Turns
$(V_1 - V_2)$	7 V	MS 9x7x4.5W - 13 Turns	MS 10x7x4.5W - 9 Turns	MS 12x8x4.5W - 7 Turns
	9 V	MS 9x7x4.5W - 17 Turns	MS 12x8x4.5W - 9 Turns	MS 15x10x4.5W - 7 Turns



Toshiba America Elec. Comps. Advanced Materials Div. 290 Donald Lynch Blvd. STE 302 Marlborough, MA 01752 (508)303-5041 FAX(508)481-8890

The information contained in this document is believed to be accurate and reliable but is presented without guarantee or warranty on the part of Toshiba. Further, nothing present herein should be interpreted as an authorization or inducement to practice any patented invention without an appropriate license